


ECE 581 Homework 2

Fall 2021

Chuck Faber

Problem 1.

 - 1) Write the SV code for the following Moore FSM. Write a testbench for it. Test your code with a simulator. Give all the codes and the simulated results.



Moore FSM Code

```
module mooreFSM (
    input in, rst, clk,
    output logic [3:0] out
);
typedef enum logic [1:0] {S0, S1, S2, S3} states_t;
states_t cs, ns;

// Sequential Logic
always_ff @(posedge clk, posedge rst) begin: set_ns
    if (rst) cs <= S0;
    else cs <= ns;
end: set_ns

// Next State Logic
always_comb begin: ns_logic
    ns = cs;
    unique case (cs)
        S0: begin
            if (in) ns = S1;
            if (!in) ns = S0;
        end
        S1: begin
            if (in) ns = S1;
            if (!in) ns = S2;
        end
        S2: begin
            if (in) ns = S3;
            if (!in) ns = S2;
        end
        S3: begin
            if (in) ns = S3;
            if (!in) ns = S0;
        end
        default: ns = cs;
    endcase
end: ns_logic

// Output Logic
```

```


always_comb begin: output_logic
    unique case (cs)
        S0: out = 4'b0000;
        S1: out = 4'b1001;
        S2: out = 4'b1100;
        S3: out = 4'b1111;
        default: out = 'x;
    endcase
end: output_logic

endmodule

```

* Testbench and Transcript for both FSMs included with part 2 of this problem below.

 - 2) Write the SV code for the following Mealy FSM. Write a testbench for it. Test your code with a simulator. Give all the codes and the simulated results.



Mealy FSM Code

```

module mealyFSM (
    input in, rst, clk,
    output logic [3:0] out
);
typedef enum logic [1:0] {S0, S1, S2, S3} states_t;
states_t cs, ns;

// Sequential Logic
always_ff @(posedge clk, posedge rst) begin: set_ns
    if (rst) cs <= S0;
    else cs <= ns;
end: set_ns

// Next State Logic
always_comb begin: ns_logic
    ns = cs;
    unique case (cs)
        S0: begin
            if (in) ns = S1;
            if (!in) ns = S0;
        end
        S1: begin
            if (in) ns = S1;
            if (!in) ns = S2;
        end
        S2: begin
            if (in) ns = S3;
            if (!in) ns = S2;
        end
        S3: begin

```

```

        if (in) ns = S3;
        if (!in) ns = S0;
    end
    default: ns = cs;
endcase
end: ns_logic

// Output Logic
always_comb begin: output_logic
    out = 'x;
    unique case (cs)
        S0: begin
            if (in) out = 4'b1001;
            if (!in) out = 4'b0000;
        end
        S1: begin
            if (in) out = 4'b1001;
            if (!in) out = 4'b1100;
        end
        S2: begin
            if (in) out = 4'b1111;
            if (!in) out = 4'b1100;
        end
        S3: begin
            if (in) out = 4'b1111;
            if (!in) out = 4'b0000;
        end
        default: out = 'x;
    endcase
end: output_logic

endmodule

```

Moore and Mealy Testbench

```

module top();

    logic in, rst, clk;
    logic [3:0] trace;
    logic [3:0] out_moore, out_mealy;

    initial begin
        clk = 1'b1;
        forever #50 clk = ~clk;
    end

    mooreFSM moore (
        .out(out_moore),
        .* );

    mealyFSM mealy (
        .out(out_mealy),
        .* );

    task resetFSM();
        in = 1'bx;
    endtask
endmodule

```

```

        @(negedge clk) rst = 1'b1;
        @(negedge clk) rst = 1'b0;
        $display("\nResetting FSM.");
    endtask

    initial begin
        for (int i = 0; i < 16; i++) begin
            resetFSM();
            trace = i & 4'hF;
            $display($time, " Trace: %04b\tInput: %01b\tMoore State: %s\tMoore Output:%04b\tMealy State:
%s\tMealy Output: %04b", trace, in, moore.cs.name(), out_moore, mealy.cs.name(), out_mealy);
            for (int j = 0; j < 4; j++) begin
                repeat (1) @(negedge clk);
                in = trace[j];
                repeat (1) @(negedge clk);
                $display($time, " Trace: %04b\tInput: %01b\tMoore State: %s\tMoore Output:%04b\tMealy
State: %s\tMealy Output: %04b", trace, in, moore.cs.name(), out_moore, mealy.cs.name(), out_mealy);
            end
        end
        $finish;
    end
endmodule

```

Moore and Mealy Transcript

```

$ vsim -c top
Reading pref.tcl

# 2020.1

# vsim -c top
# Start time: 23:21:10 on Oct 27,2021
# Loading sv_std.std
# Loading work.top
# Loading work.mooreFSM
# Loading work.mealyFSM
VSIM 1> run -all
#
# Resetting FSM.
#      150 Trace: 0000      Input: x      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: xxxx
#      350 Trace: 0000      Input: 0      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: 0000
#      550 Trace: 0000      Input: 0      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: 0000
#      750 Trace: 0000      Input: 0      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: 0000
#      950 Trace: 0000      Input: 0      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: 0000
#
# Resetting FSM.
#      1150 Trace: 0001      Input: x      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: xxxx
#      1350 Trace: 0001      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#      1550 Trace: 0001      Input: 0      Moore State: S2 Moore Output:1100      Mealy State: S2 Mealy Output: 1100
#      1750 Trace: 0001      Input: 0      Moore State: S2 Moore Output:1100      Mealy State: S2 Mealy Output: 1100
#      1950 Trace: 0001      Input: 0      Moore State: S2 Moore Output:1100      Mealy State: S2 Mealy Output: 1100
#
# Resetting FSM.
#      2150 Trace: 0010      Input: x      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: xxxx
#      2350 Trace: 0010      Input: 0      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: 0000
#      2550 Trace: 0010      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#      2750 Trace: 0010      Input: 0      Moore State: S2 Moore Output:1100      Mealy State: S2 Mealy Output: 1100
#      2950 Trace: 0010      Input: 0      Moore State: S2 Moore Output:1100      Mealy State: S2 Mealy Output: 1100
#
# Resetting FSM.
#      3150 Trace: 0011      Input: x      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: xxxx
#      3350 Trace: 0011      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#      3550 Trace: 0011      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#      3750 Trace: 0011      Input: 0      Moore State: S2 Moore Output:1100      Mealy State: S2 Mealy Output: 1100
#      3950 Trace: 0011      Input: 0      Moore State: S2 Moore Output:1100      Mealy State: S2 Mealy Output: 1100

```

[illegible]

```

#           14750 Trace: 1110      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#           14950 Trace: 1110      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#
# Resetting FSM.
#           15150 Trace: 1111      Input: x      Moore State: S0 Moore Output:0000      Mealy State: S0 Mealy Output: xxxx
#           15350 Trace: 1111      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#           15550 Trace: 1111      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#           15750 Trace: 1111      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#           15950 Trace: 1111      Input: 1      Moore State: S1 Moore Output:1001      Mealy State: S1 Mealy Output: 1001
#
# ** Note: $finish      : problem1.sv(156)
#      Time: 15950 ps  Iteration: 1  Instance: /top
# End time: 23:21:10 on Oct 27,2021, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0

```




Discussion: In my testbench, I test all combinations of 4 bit long traces, resetting both FSMs at the conclusion of each trace. I tested both FSMs simultaneously with one testbench.

In my case statements, particularly in the Mealy output logic and the next state logic for both FSMs, I check for 'in' and '!in' rather than using an if/else or ternary operator, because it is possible for 'in' to be neither '1' nor '0' (i.e. 'x' or 'z'). An if/else would catch if 'in' were '1' and in all other cases execute the 'else' statement which would not be correct behavior.


I adjust for this by initializing certain variables before using the case statement. For example, with the 'out' variable in the Mealy machine, it is initialized to 'x's before assigning to it using the unique case statement. Similarly I pre-assign the 'ns' (next state) variable with the 'cs' (current state) before assigning to it.

In addition, in every case I also provide a default case to avoid warnings when simulating when the case expression doesn't match one of the case statements (i.e. if it is 'x').


Problem 2. Convert the following Mealy Machine into an equivalent Moore Machine.

   

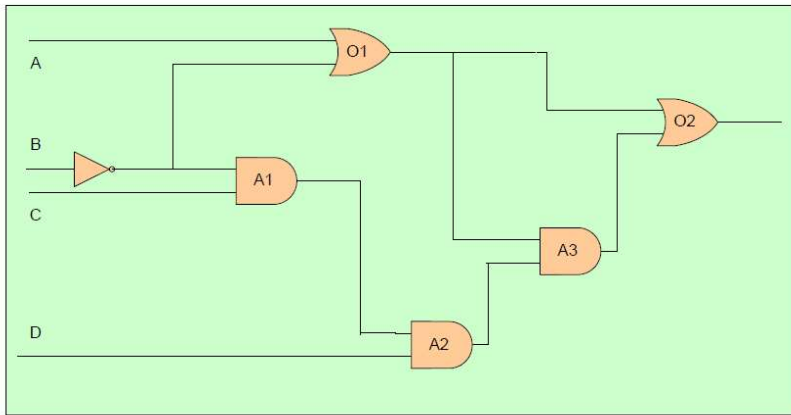Problem 3. Assume that each gate has a delay t . Find the maximal propagation delay of the circuit. Justify your result.




The maximal propagation delay is $4t$. The critical path is determined by the 'b' input. In the case of 'b' being 0, this would make the first OR gate output '1' regardless of what 'a' is. So theoretically, we wouldn't have to wait for the input of 'a' (though in this case, the input of 'b' happens at t_1 , so 'a' would already have a valid input at the gate by that time. If 'a' was 0, we would need to wait on the output of the inverter coming from 'b' to see what the output of the OR gate is. Since the first OR gate is a '1' this necessitates that the second OR gate is also a '1' while we don't care about the results from the bottom half of this circuit, so it only takes $3t$ to propagate the signal.

 


In the case of 'b'='1' we have to consider what happens with 'a'. If 'a' is '1' at t_0 , then it doesn't need to wait on the output from the inverter, and can begin to propagate a '1' all the way to the end within $2t$.

Case $b=1, a=1$

 

However in the case where 'a' is '0', the OR gate at the top must wait on the output of the inverter to determine if the output is a '0' or a '1'. Since we said 'b' is '1', the output of the inverter will be 0, and the output of the first OR gate will be 0. The second OR gate must wait on the output of the last AND gate at t_2 . By t_2 , the bottom branch is only at the second AND gate, however because the last AND gate gets a '0' at t_2 , the output of the final AND is locked to be '0' and we don't need to wait on the output from the second AND gate to propagate this change. So the final OR gate gets two '0's at t_3 , and can finally output '0' by t_4 . This is why the propagation delay is $4t$.

Case $b=1, a=0$

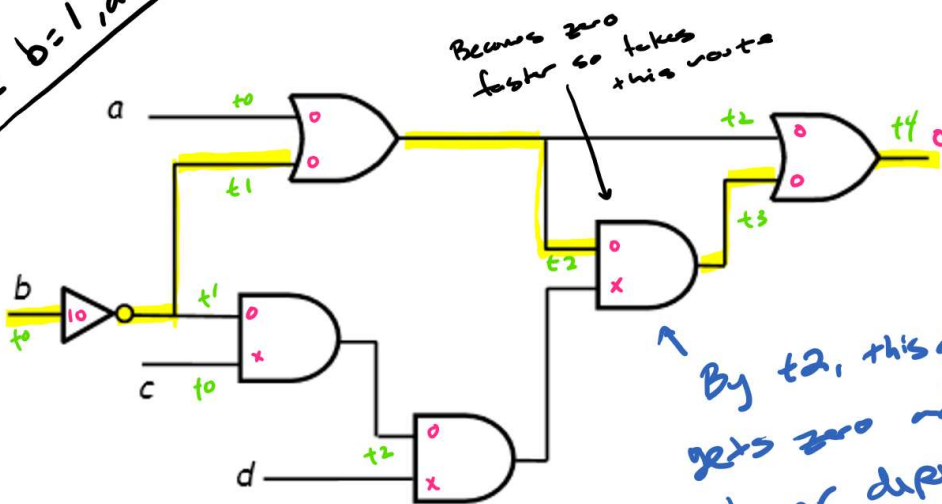

Because zero is faster so takes this route

By t_2 , this gate gets zero and the signal no longer depends on the bottom branch.