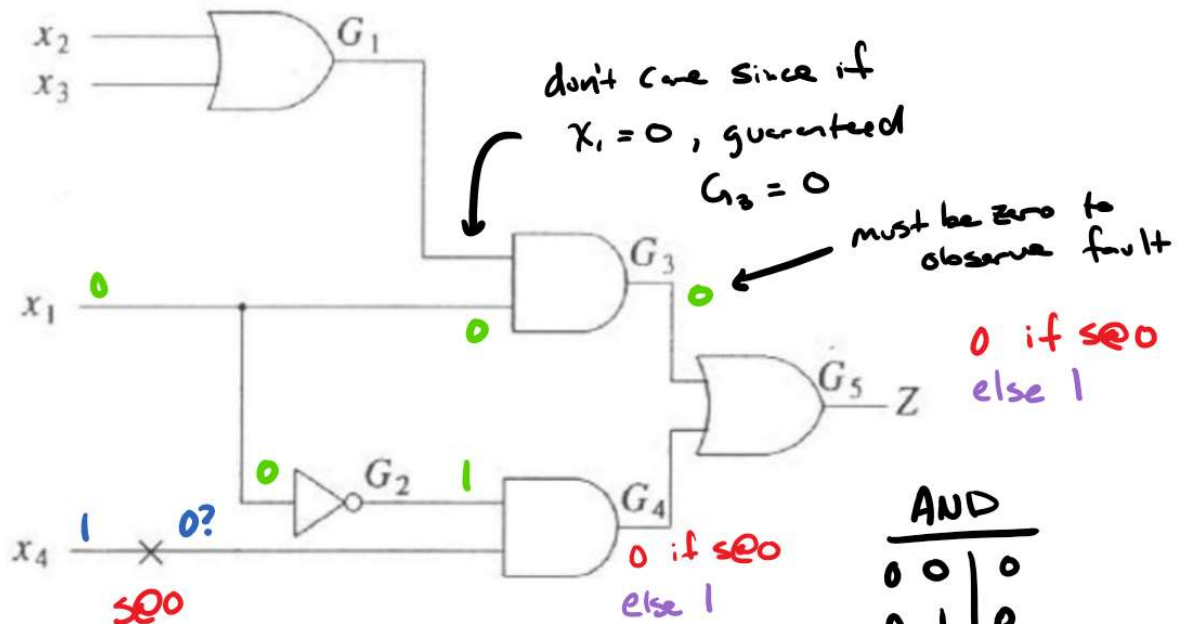


ECE 581 Homework 4

Chuck Faber

Problem 1.

For the following circuit, use the path sensitization approach, derive all the possible input patterns for detecting s-a-0 at x_4 .



$$x_4 = 1$$

$$(G_2 = 1 \ \& \ x_4 = 1) = 1$$

$$\text{if } s-a-0 \rightarrow G_4 = 0$$

Input vectors (x_1, x_2, x_3, x_4)
0 x x 1

Possible Input Vectors for detecting s-a-0:

$$\{x_1, x_2, x_3, x_4\} =$$

0001


0011

0101

0111

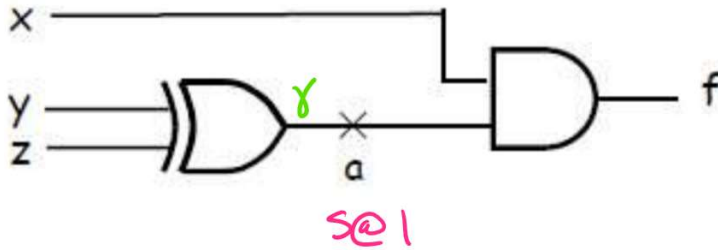Problem 2.

For the following circuit, use the Boolean difference method to determine all the input test vectors to detect the s-a-1 at a.



$$\gamma = 0 \quad \text{where} \quad \gamma = y \oplus z$$

$$\bar{\gamma} \wedge \frac{df}{d\gamma} = 1$$

$$f = x(y \oplus z) = x\gamma$$

$$\frac{df}{d\gamma} = f_{\gamma} \oplus f_{\bar{\gamma}}$$

$$f_{\gamma} = x \quad f_{\bar{\gamma}} = 0$$

$$\gamma(x \oplus 0) = 1$$

$$\gamma(x) = 1$$

$$(y \oplus z)x = 1$$

$$(\bar{y}z + y\bar{z})x = 1$$

$$x\bar{y}z + xy\bar{z} = 1$$

$$\underline{101} \quad \underline{110}$$

Input Vectors to test for s-a-1:

$\{x, y, z\} =$

101

110